

1 Introduction

In this lab, we were tasked with creating a three-part circuit: the first part is a circuit that eliminates the mechanical chatter inherent to buttons and switches; the second part is a circuit that detects the positive edge of a signal; and the third part is a counter that feeds into the seven-segment display that we programmed last lab. The final behavior of this design is the following: the user pushes a button and the count on the seven-segment display increments by one.

2 Debounce Circuit

To achieve the desired effect of eliminating the mechanical chatter of a signal, the design called for shifting in the value of the signal in question every millisecond (timed using a clock counter/pulse generator) into a register that is ten bits wide. This will ensure that the signal is stable for ten milliseconds. Every D-flip-flop inside this register is then passed through a bitwise AND gate which is then the output of the positive-edge detector.

3 Positive Edge Detector

The positive-edge detector circuit (PED circuit) is used to output a one clock-wide pulse whenever the input signal experiences a rising edge. The input to the PED circuit is the signal in question. The circuit consists of two D-flip-flops, with the signal connected to the input of the first flop, and the output of the first flop connected to the input of the second flop. The PED circuit output is then calculated as follows:

$$\text{ped_out} = Q_1 \cdot \overline{Q_2}$$

This ensures that `ped_out` is only one clock wide and fires when the input is high.

4 Counter and Seven-Segment Display

The final part of this lab was to connect the output of the PED circuit to a counter. The counter is 32 bits wide (to match with the input of the seven-segment display). It is incremented once and only once every time the button is pushed thanks to the PED circuit. The output of the counter is given to the input of the seven-segment display.