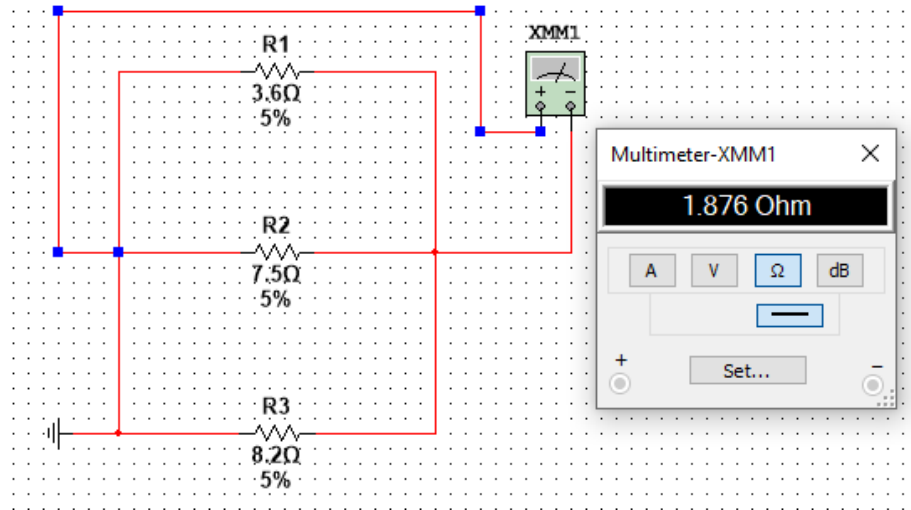


### Question 1




This multimeter reads 1.876 Ω. This is because it is reading the resistances of the three resistors (from top to bottom:  $R_1 = 3.600\ \Omega$ ,  $R_2 = 7.500\ \Omega$ , and  $R_3 = 8.200\ \Omega$ ) that are in parallel. The formula to calculate the effective value of all three resistors is as follows:

$$R_{\text{net}} = \left( \sum_{i=1}^n \frac{1}{R_i} \right)^{-1} \quad (1)$$

Using formula (1) with the above values for  $R_1$ ,  $R_2$ , and  $R_3$  gives us the following result:

$$\begin{aligned} R_{\text{net}} &= \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \\ &= \left( \frac{1}{3.600\ \Omega} + \frac{1}{7.500\ \Omega} + \frac{1}{8.200\ \Omega} \right)^{-1} \\ &= (0.278\ \Omega^{-1} + 0.133\ \Omega^{-1} + 0.122\ \Omega^{-1})^{-1} \\ &= (0.533\ \Omega^{-1})^{-1} \\ &= 1.876\ \Omega \end{aligned}$$


## Question 2

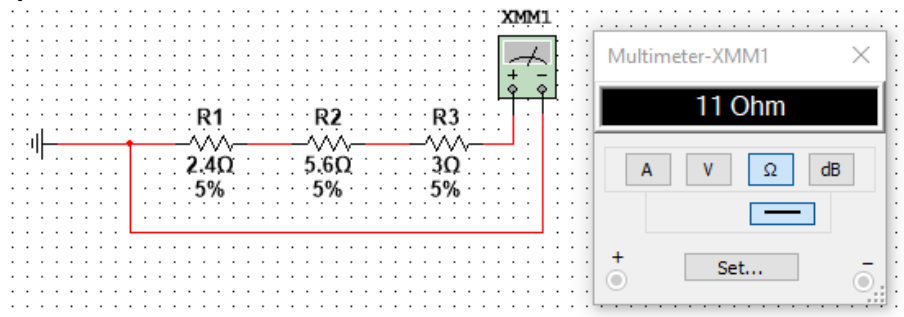

This multimeter reads 11 Ω. This is because the three resistors are connected in series ( $R_1 = 2.4\ \Omega$ ,  $R_2 = 5.6\ \Omega$ , and  $R_3 = 3.0\ \Omega$ ). When resistors are connected in series, the equivalent resistance is simply the sum of all the resistances:  $R_{\text{net}} = \sum_{i=1}^n R_i$ .

$$\begin{aligned} R_{\text{net}} &= R_1 + R_2 + R_3 \\ &= 2.4\ \Omega + 5.6\ \Omega + 3.0\ \Omega \\ &= 11\ \Omega \end{aligned}$$

## Question 3

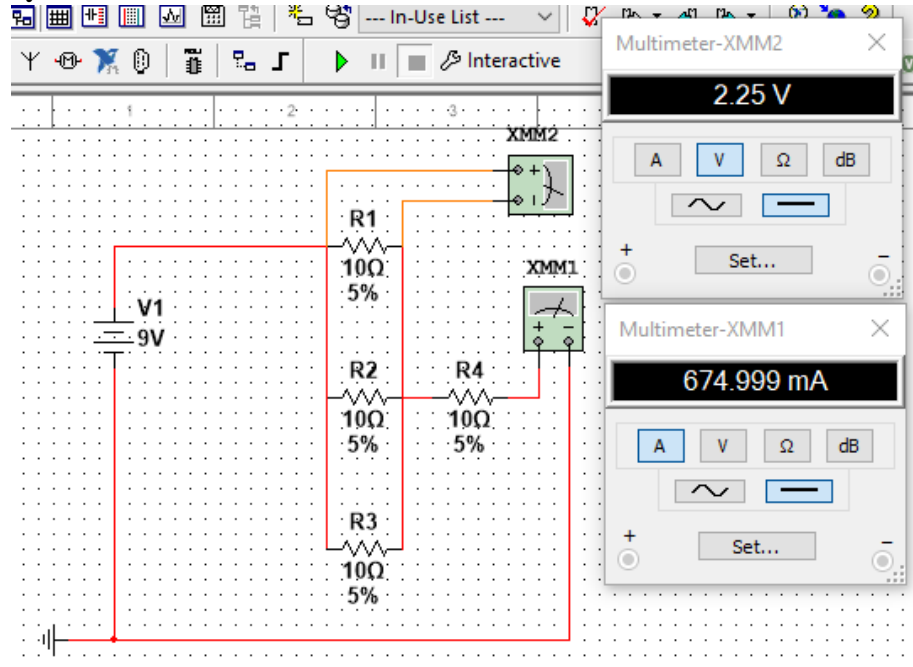

In this example, XMM1 (reading current) reads 674.999 mA (which can be rounded up to 675.000 mA, or 0.675 A) and XMM2 (reading voltage) reads

2.25 V. To calculate these values, it is first necessary to calculate the total effective resistance  $R_{\text{net}}$ . In this complex example, three resistors ( $R_1 = R_2 = R_3 = 10\ \Omega$ ) are placed in parallel with each other, while one more resistor ( $R_4 = 10\ \Omega$ ) is placed in series with the other three. First, it is required to calculate the effective total resistance of  $R_1$ ,  $R_2$ , and  $R_3$  together; next, this intermediate value can be added to  $R_4$  to achieve total resistance.

$$\begin{aligned} R_{1+2+3} &= \left( \sum_{i=1}^n \frac{1}{R_i} \right)^{-1} = \left( \sum_{i=1}^3 \frac{1}{10\ \Omega} \right)^{-1} \\ &= \left( 3 \times \frac{1}{10\ \Omega} \right)^{-1} = \left( \frac{3}{10\ \Omega} \right)^{-1} \\ &= 3.33\ \Omega \end{aligned}$$

$$\begin{aligned} R_{\text{net}} &= R_{1+2+3} + R_4 \\ &= 3.33\ \Omega + 10\ \Omega \\ &= 13.33\ \Omega \end{aligned}$$

With this quantity, we can determine the values displayed on XMM1 and XMM2.


XMM1 is reading the current going through the whole circuit, because it is connected to the very end, where there are no nodes or separations. This makes it possible to use Ohm's Law to calculate the current going through the whole circuit easily.

$$\begin{aligned} V &= IR \\ I &= \frac{V}{R} = \frac{V_s}{R_{\text{net}}} \\ &= \frac{9\ \text{V}}{13.33\ \Omega} \\ &= 0.675\ \text{A} = 675\ \text{mA} \end{aligned}$$

XMM2 is reading the voltage going across  $R_1$ ,  $R_2$ , and  $R_3$ , which are connected in parallel. We can combine these three resistances into a single equivalent resistance (the quantity  $R_{1+2+3}$ , which was calculated earlier), and then use Ohm's Law to solve for the voltage going through all three resistors.

$$\begin{aligned} V &= IR \\ V_{R_{1+2+3}} &= I_{\text{net}} \cdot R_{1+2+3} \\ &= 0.675\ \text{A} \cdot 3.33\ \Omega \\ &= 2.25\ \text{V} \end{aligned}$$

#### Question 4

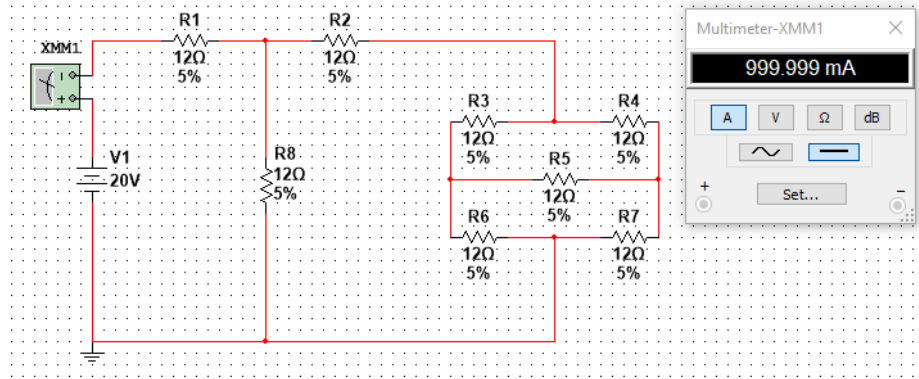

Using Ohm's Law, the equivalent resistance for this resistor network can be found algebraically if and only if both the total voltage and the total current are known for the entire circuit. The total voltage is 20 V, and the total current (as given by XMM1) is 999.999 mA, or 1 A.

$$\begin{aligned}
 V &= IR \Rightarrow R = V/I \\
 R_{\text{net}} &= \frac{V_s}{I_{\text{net}}} \\
 &= \frac{20 \text{ V}}{1 \text{ A}} \\
 &= 20 \Omega
 \end{aligned}$$

#### Question 5

##### Problem 1

$R_3 = 20 \Omega$  and  $R_4 = 20 \Omega$  are connected in parallel, while  $R_1 = 10 \Omega$  and  $R_2 = 15 \Omega$  are connected in series with  $R_3 + R_4$ . This means that it is necessary to calculate  $R_{3+4}$  before adding it to  $R_1$  and  $R_2$ .

$$\begin{aligned}
 R_{3+4} &= \left( \sum_{i=3}^4 \frac{1}{R_i} \right)^{-1} \\
 &= \left( 2 \times \frac{1}{20 \Omega} \right)^{-1} = \left( \frac{1}{10 \Omega} \right)^{-1} \\
 &= 10 \Omega
 \end{aligned}$$

$$\begin{aligned}
 R_{\text{net}} &= R_1 + R_2 + R_{3+4} \\
 &= 10 \Omega + 15 \Omega + 10 \Omega \\
 &= 35 \Omega
 \end{aligned}$$

The equivalent resistance is 35  $\Omega$ .

*Problem 2*

In this problem,  $R_7 = 20\ \Omega$  and  $R_8 = 15\ \Omega$  are connected in parallel, and this combo  $R_{7+8}$  is connected in series with  $R_5 = 7.5\ \Omega$ .

$$\begin{aligned} R_{\text{net}} &= R_5 + R_{7+8} \\ &= 7.5\ \Omega + \left( \frac{1}{20\ \Omega} + \frac{1}{15\ \Omega} \right)^{-1} \\ &= 7.5\ \Omega + (0.05\ \Omega^{-1} + 0.067\ \Omega^{-1})^{-1} \\ &= 7.5\ \Omega + (0.117\ \Omega^{-1})^{-1} \\ &= 7.5\ \Omega + 8.55\ \Omega \\ &= 16.047\ \Omega \end{aligned}$$

The equivalent resistance is  $16.047\ \Omega$ .

*Problem 3*

The resistors in this network are situated such that  $R_{13}$  and the rest of the resistors (which I will call  $R_a$ ) are connected in parallel.  $R_a$  consists of  $R_{10}$  and  $R_{11}$  in parallel plus  $R_6$  and  $R_{12}$  in parallel plus  $R_9$  in series.

$$\begin{aligned} R_{\text{net}} &= \left( \frac{1}{R_{13}} + (R_a)^{-1} \right)^{-1} \\ &= \left( \frac{1}{R_{13}} + \left( \left( \frac{1}{R_{10}} + \frac{1}{R_{11}} \right)^{-1} + \left( \frac{1}{R_6} + \frac{1}{R_{12}} \right)^{-1} + R_9 \right)^{-1} \right)^{-1} \\ &= \left( \frac{1}{10\ \Omega} + \left( \left( \frac{1}{10\ \Omega} + \frac{1}{15\ \Omega} \right)^{-1} + \left( \frac{1}{6.8\ \Omega} + \frac{1}{13\ \Omega} \right)^{-1} + 5.1\ \Omega \right)^{-1} \right)^{-1} \\ &= \left( 0.1\ \Omega^{-1} + (6\ \Omega + 4.465\ \Omega + 5.1\ \Omega)^{-1} \right)^{-1} \\ &= (0.1\ \Omega^{-1} + 0.0642\ \Omega^{-1})^{-1} \\ &= 6.088\ \Omega \end{aligned}$$

The equivalent resistance is  $6.088\ \Omega$ .

*Problem 4*

Here,  $R_{14} = 100\,\Omega$  and  $R_{17} = 100\,\Omega$  are in series, and  $R_{15} = 100\,\Omega$  and  $R_{17} = 100\,\Omega$  are in series, and these two groups are connected in parallel with  $R_{19} = 100\,\Omega$ .

$$\begin{aligned} R_{\text{net}} &= (R_{14} + R_{17}) \parallel R_{19} \parallel (R_{15} + R_{18}) \\ &= (100\,\Omega + 100\,\Omega) \parallel 100\,\Omega \parallel (100\,\Omega + 100\,\Omega) \\ &= 200\,\Omega \parallel 100\,\Omega \parallel 200\,\Omega \\ &= \frac{1}{\frac{1}{200\,\Omega} + \frac{1}{100\,\Omega} + \frac{1}{200\,\Omega}} \\ &= \frac{1}{0.005\,\Omega^{-1} + 0.01\,\Omega^{-1} + 0.005\,\Omega^{-1}} \\ &= \frac{1}{0.02\,\Omega^{-1}} = 50\,\Omega \end{aligned}$$

The equivalent resistance is  $50\,\Omega$ .