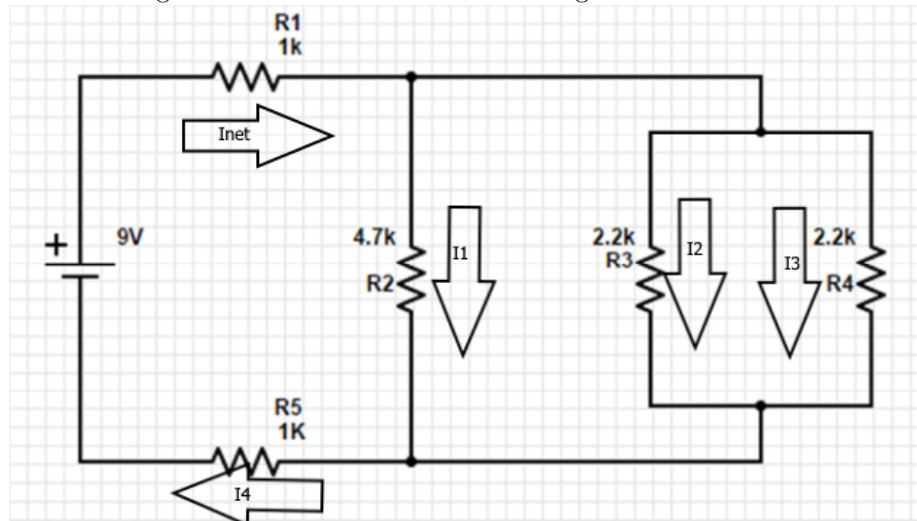


Here is a diagram of the circuit we will be solving:



The given values for this circuit are as follows:

$$\begin{aligned} V_s &= 9 \text{ V} \\ R_1 &= 1 \text{ k}\Omega \\ R_2 &= 4.7 \text{ k}\Omega \\ R_3 &= R_4 = 2.2 \text{ k}\Omega \\ R_5 &= 1 \text{ k}\Omega \end{aligned}$$

The equivalent resistance for this circuit can be calculated as follows:

$$\begin{aligned} R_{\text{net}} &= R_1 + ((R_3 \parallel R_4) \parallel R_2) + R_5 \\ &= 1 \text{ k}\Omega + ((2.2 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega) \parallel 4.7 \text{ k}\Omega) + 1 \text{ k}\Omega \\ &= 1 \text{ k}\Omega + (1.1 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega) + 1 \text{ k}\Omega \\ &= 1 \text{ k}\Omega + 0.891 \text{ k}\Omega + 1 \text{ k}\Omega \\ &= 2.891 \text{ k}\Omega \end{aligned}$$


Using Ohm's Law ($V = IR$), we can find the total current for the circuit:

$$\begin{aligned} I_{\text{net}} &= \frac{V_s}{R_{\text{net}}} \\ &= \frac{9 \text{ V}}{2.891 \text{ k}\Omega} = 3.113 \text{ mA} \end{aligned}$$


The amount of current going through each resistor and the amount of voltage dropped by each resistor can also be calculated using Ohm's Law.

I_{net}	3.113 mA
V_{R_1}	$3.113 \text{ mA} \times 1 \text{ k}\Omega = 3.113 \text{ V}$
V_{R_2}	$V_s - (V_{R_1} + V_{R_5}) = 9 \text{ V} - (3.113 \text{ V} + 3.113 \text{ V}) = 2.774 \text{ V}$
V_{R_3}	2.774 V
V_{R_4}	2.774 V
V_{R_5}	$3.113 \text{ mA} \times 1 \text{ k}\Omega = 3.113 \text{ V}$
I_1	$2.774 \text{ V} / 4.7 \text{ k}\Omega = 0.590 \text{ mA}$
I_2	$2.774 \text{ V} / 2.2 \text{ k}\Omega = 1.261 \text{ mA}$
I_3	$2.774 \text{ V} / 2.2 \text{ k}\Omega = 1.261 \text{ mA}$
I_4	$3.113 \text{ V} / 1 \text{ k}\Omega = 3.113 \text{ mA}$

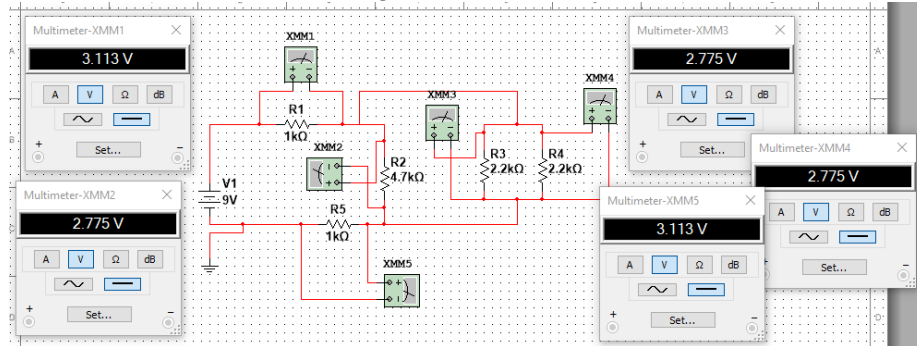
Here are all the values for voltage when simulated in Multisim:



And here are all the values for current:

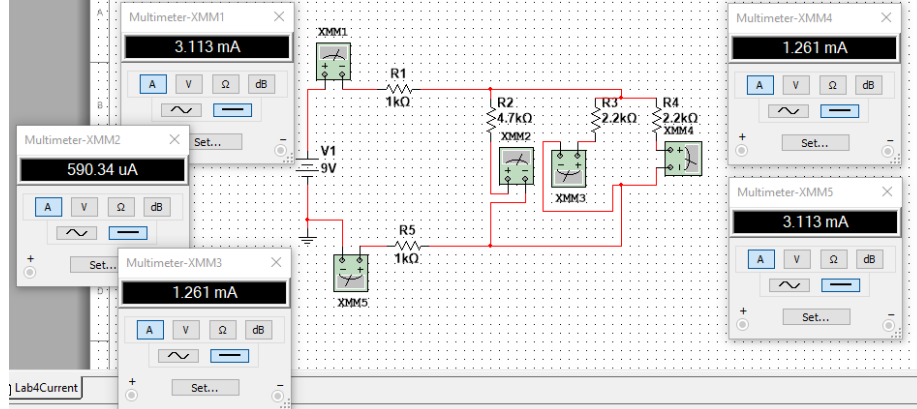

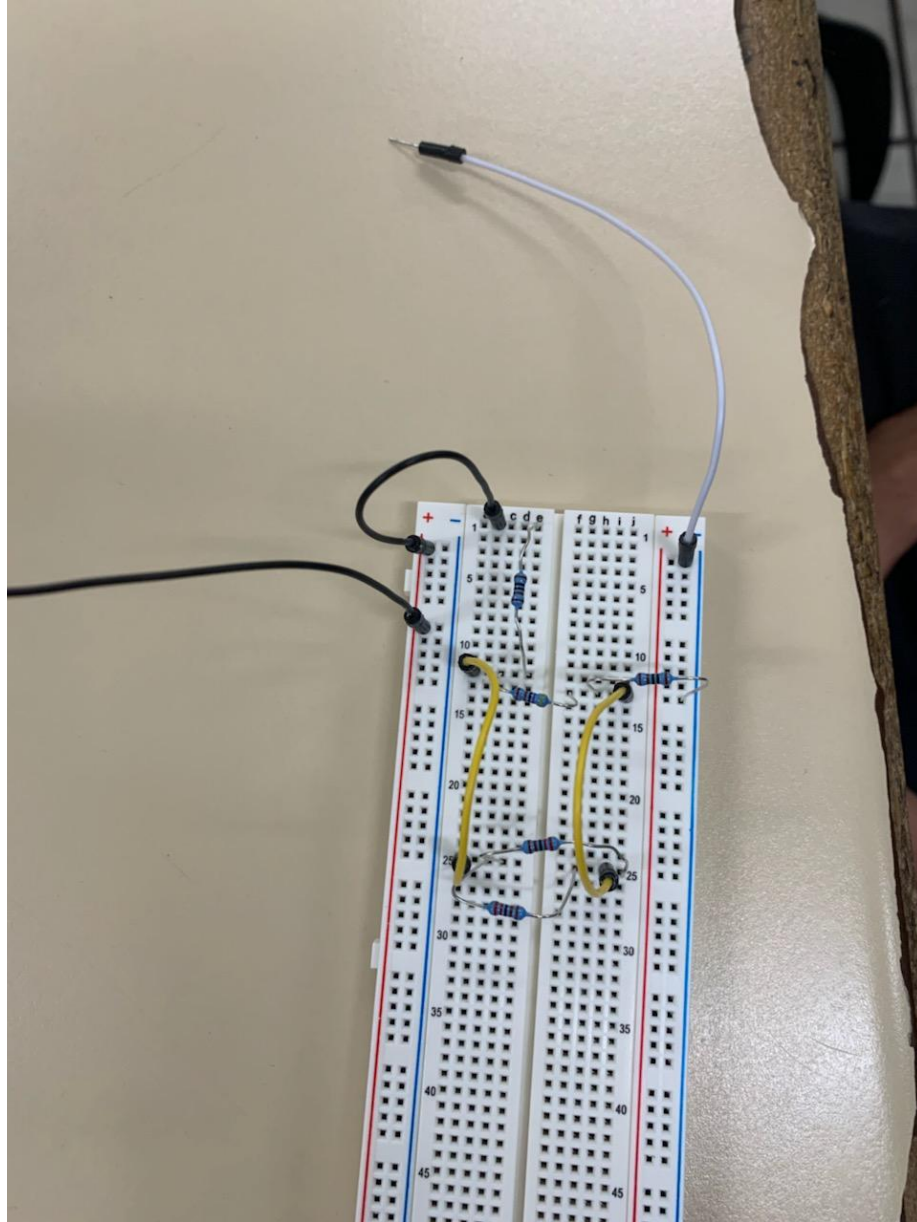Here is the physical breadboard build of this circuit:



And here are all the values I tested for using a physical digital multimeter:

R_1	$998\,\Omega$
R_2	$4.7\,\text{k}\Omega$
R_3	$2.2\,\text{k}\Omega$
R_4	$2.2\,\text{k}\Omega$
R_5	$997\,\Omega$
I_T	$3.11\,\text{mA}$
I_1	$0.60\,\text{mA}$
I_2	$1.25\,\text{mA}$
I_3	$1.25\,\text{mA}$
I_4	$3.11\,\text{mA}$
V_{R_1}	$3.11\,\text{V}$
V_{R_2}	$2.77\,\text{V}$
V_{R_3}	$2.77\,\text{V}$
V_{R_4}	$2.77\,\text{V}$
V_{R_5}	$3.11\,\text{V}$